

CAREY FOSTER's BRIDGE

A Brief Review

Shashvat Jain

November 5, 2021

OUTLINE

1. INTRODUCTION
2. THE EXPERIMENT
 - 2.1 AIM AND APPARATUS USED
 - 2.2 CIRCUIT DIAGRAM
 - 2.3 THEORY
 - 2.4 PROCEDURE
 - 2.5 OBSERVATIONS
 - 2.6 RESULTS
3. REFERENCES

1. INTRODUCTION

What is Carey Foster's bridge? Why do we need another bridge?

The Carey Foster's bridge is another modification of Wheatstone bridge arrangement used to measure relatively medium or equal resistances compared to other resistances in the arrangement. As a result it becomes a necessity to ask why do we need Carey Foster's bridge? The answer to this question must lie within the subtleties of its modification.

So let's take a closer look with an experiment using the bridge.

2. THE EXPERIMENT

AIM AND APPARATUS USED

- **AIM :** To determine an unknown low resistance using the Carey Foster's bridge.
- **APPARATUS USED :** Carey foster's bridge, unknown low resistance, Resistance box, Battery, jockey, one way key, Galvanometer, small shunt resistance, connecting wires of almost zero resistance.

CIRCUIT DIAGRAM

Carey_Foster_bridge.png

THEORY

X is the unknown resistance. P, Q and Y are known resistances of magnitude comparable to that of X, forming the other half of the bridge. The bridge wire EF has a jockey contact D placed along it and is slid until the galvanometer G measures zero. The thick-bordered areas are thick copper busbars of almost zero resistance.

The bridge is said to be balanced when no current passes through the galvanometer.

FORMULA USED

Let ℓ_1 be the length ED when X is placed on the right and α is the unknown left-side extra resistance EX and β is the unknown right-side extra resistance FY, and σ is the resistance per percent length of the bridge wire:

$$\frac{P}{Q} = \frac{X + \sigma(\ell_1 + \alpha)}{Y + \sigma(100 - \ell_1 + \beta)}$$

and add 1 to each side:

$$\frac{P}{Q} + 1 = \frac{X + Y + \sigma(100 + \alpha + \beta)}{Y + \sigma(100 - \ell_1 + \beta)} \quad (1)$$

Now swap X and Y. ℓ_2 is the new null point reading:

$$\frac{P}{Q} = \frac{Y + \sigma(\ell_2 + \alpha)}{X + \sigma(100 - \ell_2 + \beta)}$$

FORMULA USED

and add 1 to each side:

$$\frac{P}{Q} + 1 = \frac{X + Y + \sigma(100 + \alpha + \beta)}{X + \sigma(100 - \ell_2 + \beta)} \quad (2)$$

From (1) and (2) we get:

$$\begin{aligned} Y + \sigma(100 - \ell_1 + \beta) &= X + \sigma(100 - \ell_2 + \beta) \\ \implies X &= Y + \sigma(\ell_2 - \ell_1) \end{aligned} \quad (3)$$

Subtleties of Modification

- Note that the unknown unwanted resistances α and β have no affect on the finally obtained resistance X . This reduces the error in the result to a great extent. This boosts the sensitivity of the instrument
- Comparing this to a metre bridge, This setup ensures that the components of the circuit are not majorly harmed incase the unknown resistance is very small.
- This enables more accurate measurements of smaller resistances.

PROCEDURE

To find the unknown resistance(X)

1. Setup the circuit as shown in figure 1
2. Start by switching on the circuit and sliding the galvanometer jockey until the deflections become very small.
3. Now remove the shunt resistance and search for null point in the region of minimal deflection.
4. Once the null point is found, measure EF.
5. Swap X and Y and repeat the above steps to get ℓ_2 .
6. Repeat 1,2,3 and 4 with different values of Y.

To find the resistance per unit length (σ)

1. Setup the circuit as shown in circuit diagram but now replace X with a wire of zero resistance.

DATA

Data was obtained from the following lab report [\[read\]](#)

1. LC of the instrument used to measure $Y = 0.01 \Omega$
2. LC of metre scale = 0.1cm

Table 1: Observations for Resistance per unit length(σ)

S.No.	$Y(\Omega)$	$\ell_1(\text{cm})$	$\ell_2(\text{cm})$	$\ell_1 - \ell_2 (\text{cm})$	$\sigma(\Omega/\text{cm})$
-------	-------------	---------------------	---------------------	-------------------------------	----------------------------

Table 3: Observations for value of X

S.No.	$Y(\Omega)$	$\ell_1(cm)$	$\ell_2(cm)$	$\ell_2 - \ell_1 (cm)$	$X(\Omega)$
-------	-------------	--------------	--------------	------------------------	-------------

DATA ANALYSIS

- Mean value of $\sigma = 0.032 \Omega/cm$
- Error in σ due to LC ≈ 0.005
- Standard error in $\sigma = 0.002$
- Mean value of $X = 0.7 \Omega$
- Error in X due to LC ≈ 0.1
- Standard error in $X = 0.01$

RESULTS

- Value of unknown resistance $X = 0.7 \pm 0.1$

PRECAUTIONS

- Make sure that all resistances are of low and comparable magnitude. High unknown resistances can render the galvanometer and resistance wire useless.
- Do not forget to remove shunt resistance when close to the null point.
- Do not rub the jockey against the resistance wire, slide it gently.
- Make a note of the error in the measurements of the known resistances.

Light Dependent Resistances LDRs

- During the early 20th century the bridge was popularly used for measuring unknown resistances.
- Carey Foster's bridge arrangement is used in light detectors where the unknown resistance is a Light dependent resistance(LDR) whose resistance decreases with increase in the intensity of light falling on it.

3. REFERENCES

REFERENCES